 


DIGITAL DESIGN – CS223
LAB 5
REPORT

İREM SEVEN
21704269

Date: 17.04.19
Trainer Pack No: 11

Fsm Diagram for Multiplier



00 = initial state
01 = no addition
10 = addition by accumulator

SystemVerilog Code

```
module multiplier
(
    input logic clk,
    input logic reset,
    input logic in,
    input logic [6:0] B,
    input logic [6:0] M,
    output logic [7:0] out
);

typedef enum logic [1:0] {S0,S1,S2} statetype;
    statetype state, nextstate;

logic [7:0] partialB;
logic [3:0] partialM;
assign partialM = M;
logic [5:0] count;

always_ff@ (posedge clk)                                //ACCUMULATOR
begin
    if (reset == 1'b1)
        out <= 8'b0000_0000;
    else if (in == 1 && partialM[0] == 1)
        begin
            partialB = partialM[0] * B;
            out = partialB + out;
        end
    end
end

always_ff@ (posedge clk)                                //SHIFT REGISTER B 8 bit
begin
    if (reset == 1'b1)
        begin
            out = 8'b0000_0000;
            partialB <= out;
        end
    else if(in == 1'b1)
        partialB = partialB << 1;
    end
end

always_ff@ ( posedge clk)                                //SHIFT REGISTER M 4 bit
begin
    if (reset == 1'b1)
        partialM <= 8'd0000_0000;
    else if(in == 1'b1)
        partialM = partialM >> 1;
    end
end
```

```

always_ff@ (posedge clk)                                //STATE REGISTER
begin
    if (reset == 1'b1)
        state <= S0;
    else if (in == 1)
        state <= nextstate;
end

```

```

always@(posedge clk)                                    //FSM COMB
begin
    case(state)
        S0:
            begin
                if(in == 1 && partialM[0] == 1 )
                    nextstate <= S1;
                else if(in == 1 && partialM[0] == 0)
                    nextstate <= S2;
            end

        S1:
            begin
                if(in == 1 && partialM[0] == 1)
                    nextstate <= S1;
                else if(in == 1 && partialM[0] == 0)
                    nextstate <= S2;
            end

        S2:
            begin
                if(in == 1 && partialM[0] == 1)
                    nextstate <= S1;
                else if(in == 1 && partialM[0] == 0)
                    nextstate <= S2;
            end
    endcase
end

```

```

// Output Logic
always @ (posedge clk)
begin
    if (state == S0)
        out = 8'b0000_0000;
    else if (state == S1)
        out = out;
    else if (state == S2)
        out = out;
end

```

```

endmodule

```

TestBench Code

```
module Testbench();

    input logic clk,
    input logic reset,
    input logic in,
    input logic [6:0] B,
    input logic [6:0] M,
    output logic [7:0] out

    always
    begin
        clk = 0; #5; clk = 1; #5;
    end

    multiplier dut(clk, reset, in, B , M, out);

    initial begin
        #20;
        reset = 0;
        in = 1;
        M = 1001;
        B = 1111;
        #20;
        in = 0;
        #20
        in = 1;
        M = 1100;
        B = 1101;
        #20;
        reset = 1;
    end

endmodule
```